

# Technician Class Course

## Session 3



**ARRL** *The national association for*  
**AMATEUR RADIO**

# BASIC ELECTRICAL PROPERTIES




**ARRL** *The national association for*  
**AMATEUR RADIO**

# Resistors and Resistance

- Resistor: the electronic component
- Resistance: the opposition to the flow of an electric current
- Unit of resistance: Ohm
- Energy is dissipated as heat

Schematic Symbol

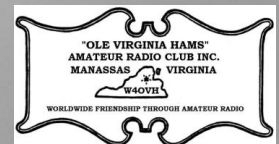

# Inductors and Inductance

- Inductor: the electronic component
- Inductance: opposition to “time-varying” (i.e., AC) current changes
- Unit of inductance: Henry
- Energy is stored in a magnetic field

Schematic Symbol



# Capacitors and Capacitance

- Capacitor: the electronic component
- Capacitance: opposition to “time-varying” (i.e., AC) voltage changes
- Unit of capacitance: Farad
- Energy is stored in an electric field

Schematic Symbol



**ARRL** The national association for  
AMATEUR RADIO




# REACTANCE, IMPEDANCE AND RESONANCE



**ARRL** *The national association for  
AMATEUR RADIO*

# Frequency and Phase Terminology

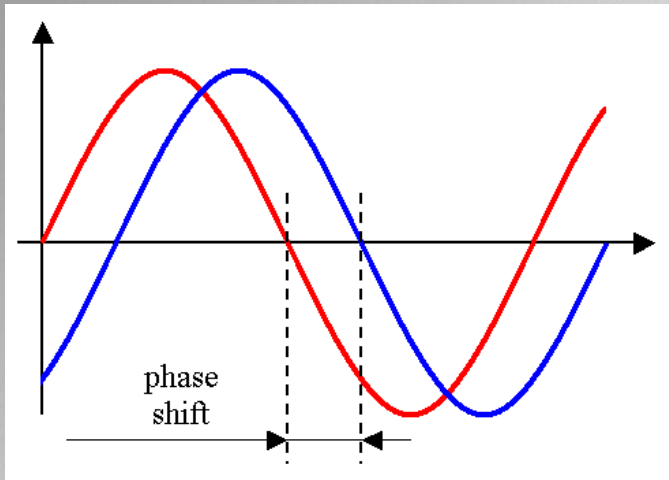

- The red and blue traces shown are out of phase
- Phase shift a is time separation

- The red trace “lags” the blue trace
- The blue trace “leads” the red trace



# Analogy between DC and AC

- Resistance (R)
  - same as what was discussed with DC



# Analogy between DC and AC

- Reactance ( $X$ ) is unique to AC circuits
  - Capacitive reactance ( $X_C$ )
    - Unit of measure: Ohm
    - Frequency dependent
  - Inductive reactance ( $X_L$ )
    - Unit of measure: Ohm
    - Frequency dependent

# Analogy between DC and AC


- In DC circuits, the current and voltage are always in phase
- In AC circuits, the current and voltage are (generally) not in phase
  - Resistive circuits – current in phase with voltage
  - Capacitive circuits – current leads voltage
  - Inductive circuits – current lags voltage



# Impedance


- Real circuits contain combinations of R, L and C
- Impedance ( $Z$ ) is the combination of the total resistance and the total reactance
  - Both capacitive and inductive reactance
- Unit of measure: Ohm

# Resistance, Reactance and Impedance

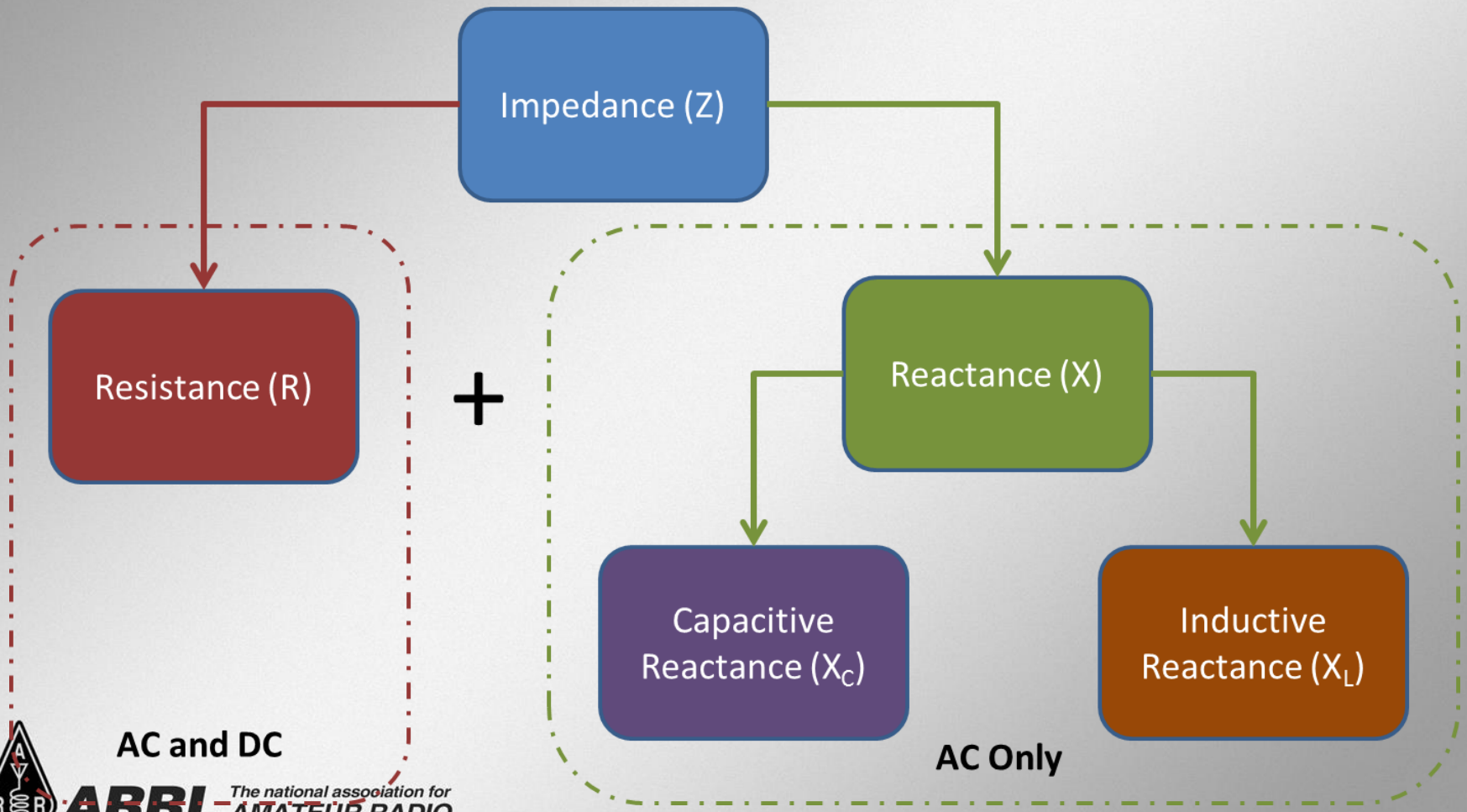
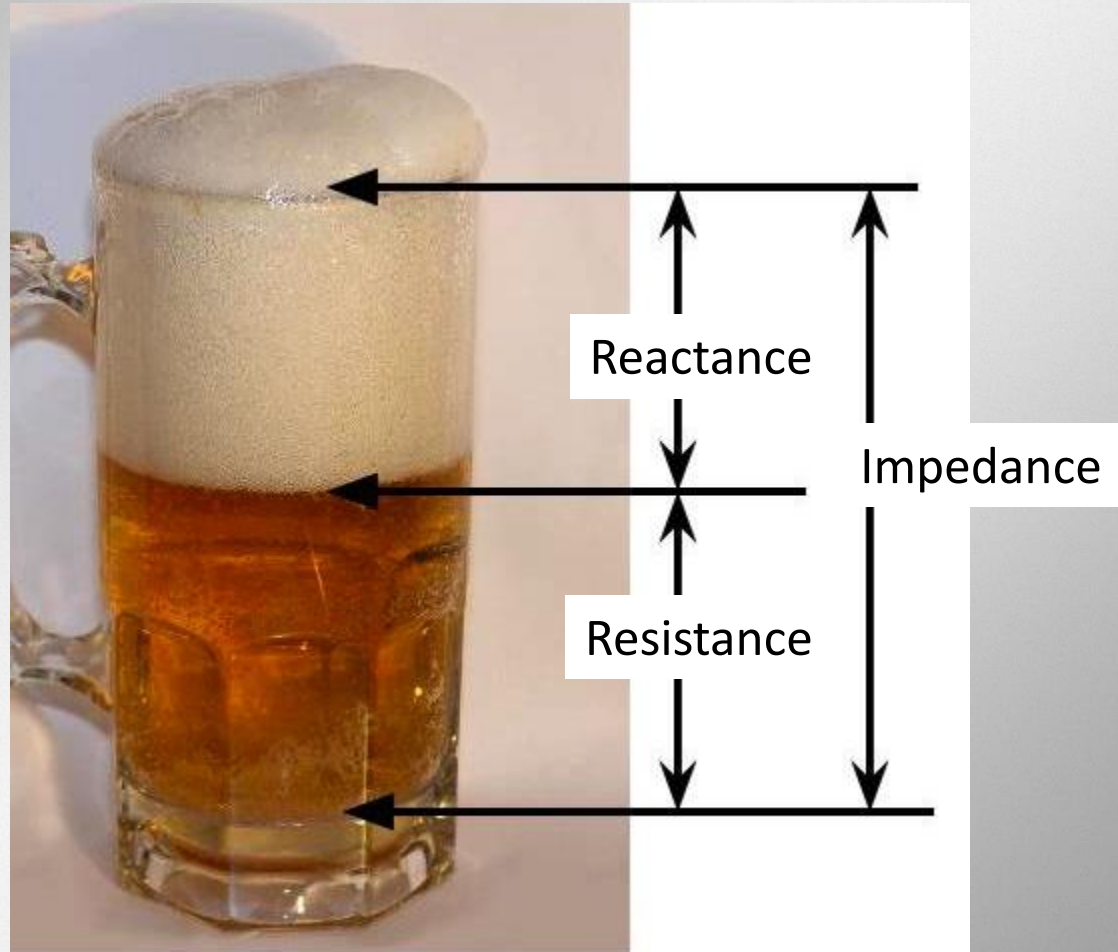
# Impedance


The power that does the work is in the resistance...



**ARRL** The national association for  
AMATEUR RADIO
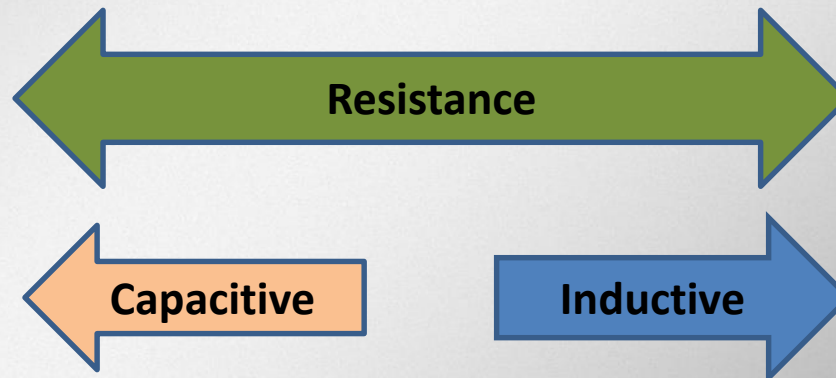
# Impedance

- Contributions from capacitive and inductive reactances work to oppose each other
- The circuit sees the net effect of the reactances but the resistances remain the same




# Resonance

- Resonance is a special condition
- Reactances are equal in amplitude but opposite in phase/sign
- Reactances cancel each other out at one specific frequency
  - This is the resonant frequency
  - Resistance remains unchanged

# Resonant Circuit Behavior


$$X_L < X_C$$

“Capacitive”

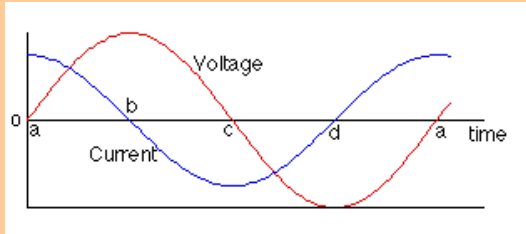



$$X_L = X_C$$

“Resonance”

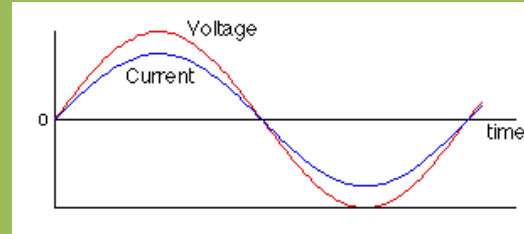

$$X_L > X_C$$

“Inductive”

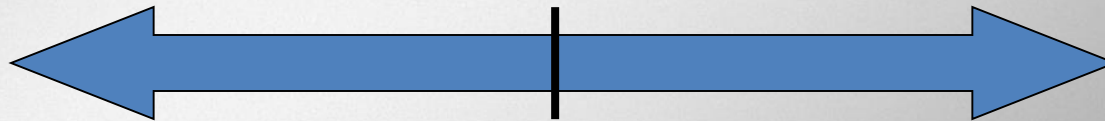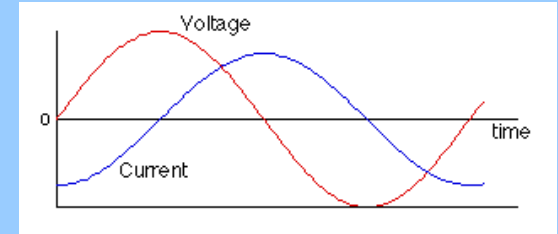

Below Resonance

Resonance

Above Resonance

**Maximum power transfer occurs at resonance**



**ARRL** The national association for  
AMATEUR RADIO





# Resonance

- Resonance is an important phenomena for radio circuits and antennas
- We “tune” circuits and antennas for resonance for the maximum transfer of power between stages and between radios and antennas

# Antennas

- Antennas also exhibit a combination of resistance and reactance
- Reactance changes with frequency
- Antennas are adjusted to be resonant at the desired frequency

